

GIST EECS

HW#2 (Digital IC)

ChangJoo Park (박창주) 20194044

2019-10-8

(1) Inverter DC analysis

```

inv.sp for SPICE3F5

.MODEL NMOS NMOS LEVEL=2 LD=0.15U TOX=200.0E-10
+ NSUB=5.36726E+15 VTO=0.743469 KP=8.00059E-05 GAMMA=0.543
+ PHI=0.6 U0=655.881 UEXP=0.157282 UCRIT=31443.8
+ DELTA=2.39824 VMAX=55260.9 XJ=0.25U LAMBDA=0.0367072
+ NFS=1E+12 NEFF=1.001 NSS=1E+11 TPG=1.0 RSH=70.00
+ CGDO=4.3E-10 CGSO=4.3E-10 CJ=0.0003 MJ=0.6585
+ CJSW=8.0E-10 MJSW=0.2402 PB=0.58
* Weff = WDrawn - Delta_W
* The suggested Delta_W is 1.9970E-07


.MODEL PMOS PMOS LEVEL=2 LD=0.15U TOX=200.0E-10
+ NSUB=4.3318E+15 VTO=-0.738861 KP=2.70E-05 GAMMA=0.58
+ PHI=0.6 U0=261.977 UEXP=0.323932 UCRIT=65719.8
+ DELTA=1.79192 VMAX=25694 XJ=0.25U LAMBDA=0.0612279
+ NFS=1E+12 NEFF=1.001 NSS=1E+11 TPG=-1.0 RSH=120.6
+ CGDO=4.3E-10 CGSO=4.3E-10 CJ=0.0005 MJ=0.5052
+ CJSW=1.349E-10 MJSW=0.2417 PB=0.64
* Weff = WDrawn - Delta_W
* The suggested Delta_W is 3.1280E-07

Vdd vdd 0 5.0
Vin in 0 0.0
M1 out in 0 0 NMOS W=2.4 L=1.2
M2 out in vdd vdd PMOS W=4.8 L=1.2

.op
.dc Vin 0 5 0.01
.print dc V(in) V(out)
.end

```

Inverter DC analysis (VIN vs VOUT)

 

→ The output voltage drops steeply when input voltage is around at 2.3V.


Vin (input Voltage)	PMOS	NMOS	Misc.
$V_{in} < V_{tn}$	Triode	Cut-off	V_{tn} : NMOS threshold voltage V_{tp} : PMOS threshold voltage
$V_{tn} < V_{in} < V_{DD}/2$	Triode	Saturation	
$V_{in} = V_{DD}/2$	Saturation	Saturation	
$V_{DD}/2 < V_{in} < V_{DD} - V_{tp} $	Saturation	Triode	
$V_{DD} - V_{tp} < V_{in}$	Cut-off	Triode	

(2) NMOSFET I-V Characteristic for drain to source node (with gate voltage variation)

```
* mosiv.sp for SPICE3F5
include models_1p2mu.sp

Vgs g 0 0
Vds d 0 0
M1 d g 0 0 NMOS W=2.4 L=1.2

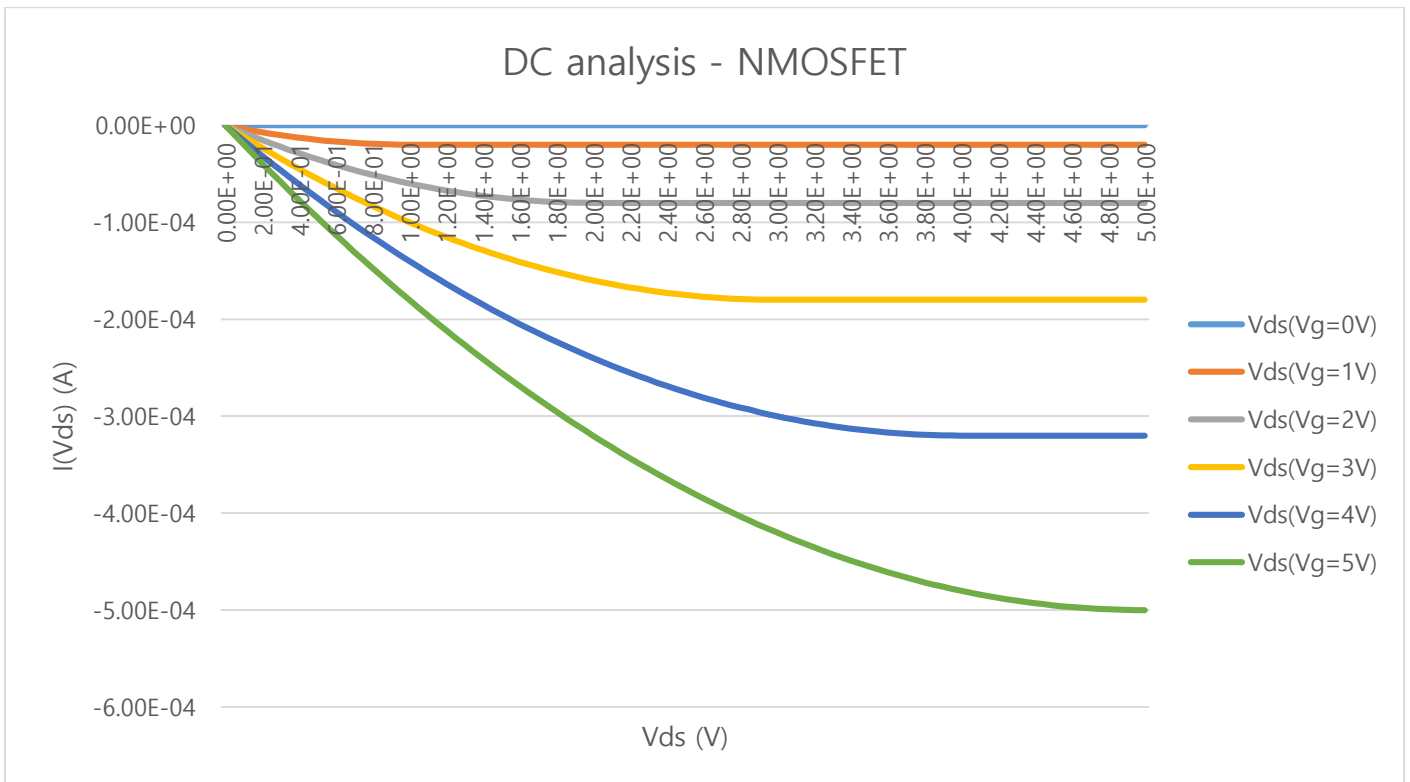
.dc Vds 0 5.0 0.05 Vgs 0 5.0 1.0
.print dc V(g) I(Vds)
.end
```



- ➔ current from drain to source node (I_{ds}) increases when voltage dropped between drain to source node (V_{ds}) increases. In addition, the current increases when gate voltage (V_{gs}) increases.
- ➔ The point where I_{ds} saturates is depend on V_{gs} . The V_{ds} value where I_{ds} saturates become smaller as V_{gs} decreases.

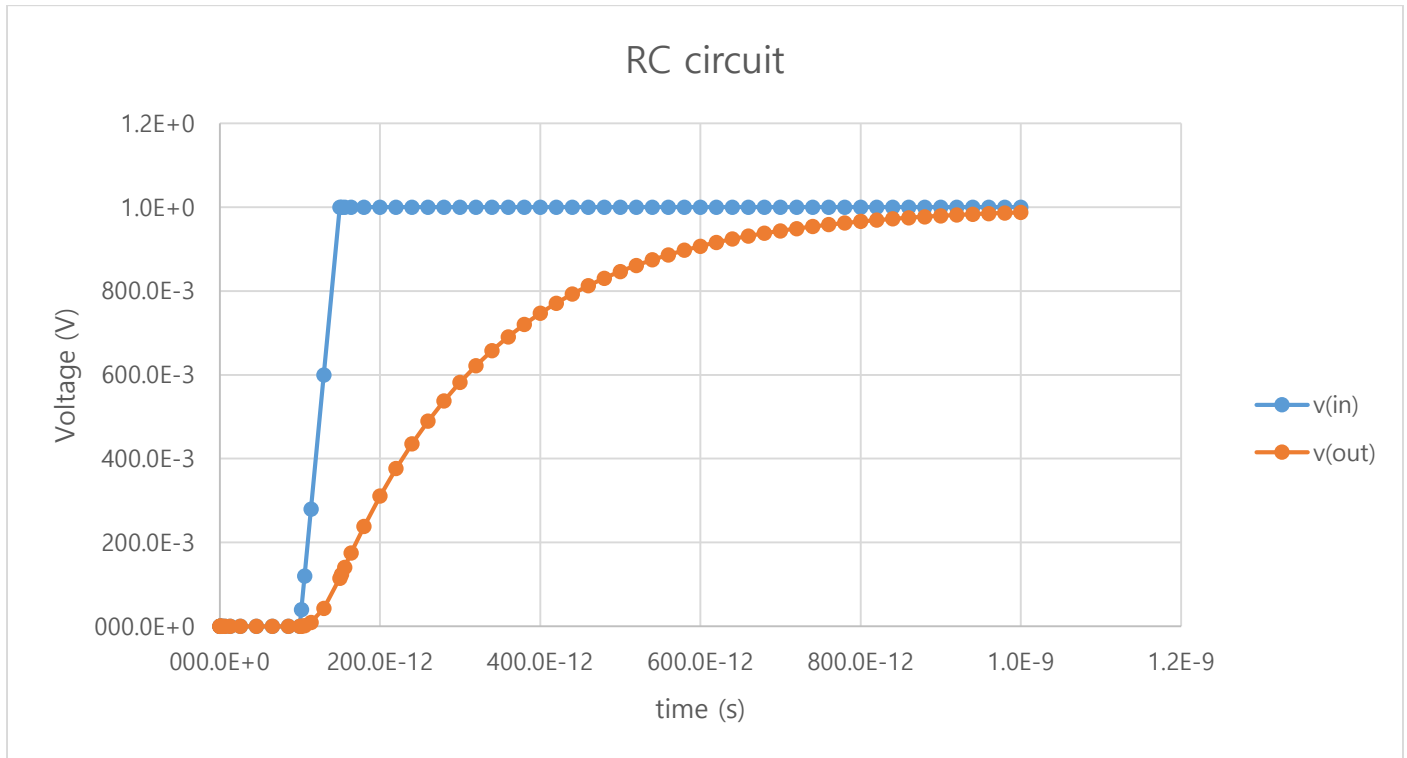(3) RC circuit (settling time)

```
* rc.sp for SPICE3F5  
  
Vin in 0 pwl 0ps 0 100ps 0 150ps 1.0 1ns 1.0  
R1 in out 2K  
C1 out 0 100f  
  
.tran 20ps 1ns  
.print tran V(in) V(out)  
.end  
~
```



- ➔ Since capacitor require few times to be charged, the output voltage of the RC circuit requires certain settling time to be equal to the input voltage.
- ➔ This is generally called "Passive Low Pass Filter (LPF)", which blocks high frequency signals, but passes low frequency ones.