

## Digital Integrated Circuits HW #3

20175138 임경록

### Exercise 2.1

Initial conditions:

$$\frac{W}{L} = \frac{4}{2} \lambda = \frac{1.2}{0.6} \mu m, t_{ox} = 100 \times 10^{-8} cm$$

$$\mu_n = 350 cm^2/V$$


$$V_t = 0.7V$$

We can divide IV characteristics in 3 states. ( $\beta = \mu_n C_{ox} \frac{W}{L} = 242 \mu A/V^2$ )

Subthreshold:  $I_d = 0$  at  $V_{gs} < V_t$

Linear region:  $I_d = \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$  at  $V_{gs} > V_t$  and  $V_{ds} < V_{gs} - V_t$

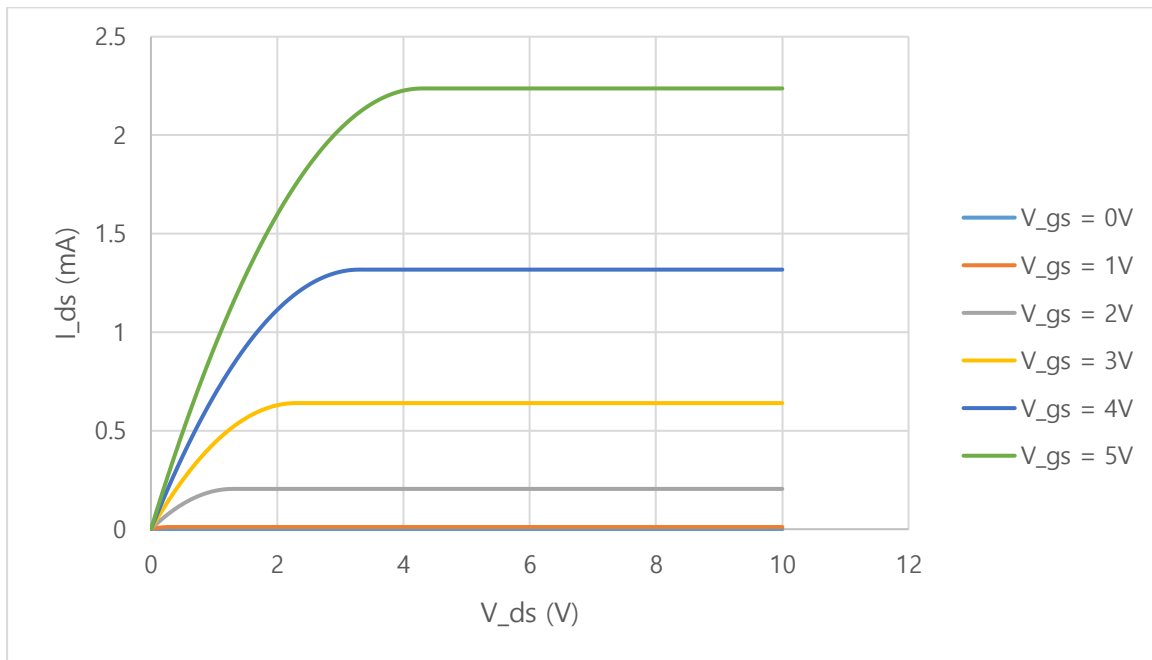Saturation region:  $I_d = \frac{\beta}{2} (V_{gs} - V_t)^2$  at  $V_{gs} > V_t$  and  $V_{ds} > V_{gs} - V_t$



### Exercise 2.2

In Fig 2.32 (a), the current is

$$I_{DS1} = \beta \left( V_{DD} - V_t - \frac{V_{DS}}{2} \right) V_{DS} \text{ --- ①}$$

In Fig 2.32 (b), the current is

$$I_{DS2} = \beta' \left( V_{DD} - V_t - \frac{V_1}{2} \right) V_1 = \beta' \left( (V_{DD} - V_1) - V_t - \frac{V_{DS} - V_1}{2} \right) (V_{DS} - V_1) \text{ --- ②}$$

$$(\beta = \mu_n C_{ox} \frac{W}{2L}, \beta' = \mu_n C_{ox} \frac{W}{L})$$

Using equation of ②, find  $V_1$  value.

$$V_1 = (V_{DD} - V_t) - \sqrt{(V_{DD} - V_t)^2 - \left( V_{DD} - V_t - \frac{V_{DS}}{2} \right) V_{DS}} \text{ --- ③}$$

(The lower transistor on (b) is in the linear region so  $V_1 < V_{DD} - V_t$  should be satisfied.

$V_1$  is not  $(V_{DD} - V_t) + \sqrt{(V_{DD} - V_t)^2 - \left( V_{DD} - V_t - \frac{V_{DS}}{2} \right) V_{DS}}$  because of  $V_1 > V_{DD} - V_t$  .)

Insert the equation of ③ in  $I_{DS2} = \beta' \left( V_{DD} - V_t - \frac{V_1}{2} \right) V_1$ .

Then,  $I_{DS2} = I_{DS1}$ .

### Exercise 2.3

The single transistor in (a) and the bottom transistor in (b) are not affected by body effect because of  $V_{sb} = 0$ . However, the threshold voltage of the top transistor in (b) would be raised because of  $V_{sb} > 0$ . Therefore, the overdrive voltage would be decreased and the current would be decreased. Therefore,  $I_{DS2} < I_{DS1}$ .

### Exercise 2.4

$$C_{permicron} = \frac{\epsilon_{ox}}{t_{ox}} L = \frac{3.9 \times 8.85 \times 10^{-14} (F/cm)}{16 \times 10^{-10} (m)} \times 90 \times 10^{-7} (cm) = 1.94 \times 10^{-9} F/m$$

### Exercise 2.5

Unit-size diffusion contact:  $4 \times 5 \lambda = 1.2 \times 1.5 \mu m$  -> Area:  $1.8 \mu m^2$ , Perimeter:  $5.4 \mu m$

$$C_{db}(at 0V) = 1.8 \times 0.42 + 5.4 \times 0.33 = 2.54 fF$$

$$C_{db}(at 5V) = 1.8 \times 0.42 \times \left(1 + \frac{5}{0.98}\right)^{-0.44} + 5.4 \times 0.33 \times \left(1 + \frac{5}{0.98}\right)^{-0.12} = 1.78 fF$$

## Drawing Potential Graph

$$I_d = WC_{ox}[V_g - V(x) - V_t]\mu_n \frac{dV(x)}{dx}$$


$$\int_0^x \frac{I_d}{\mu_n WC_{ox}} dx = \int_0^{V_x} [V_g - V(x) - V_t] dV(x)$$

$$\frac{I_d}{\mu_n WC_{ox}} x = -\frac{1}{2} (V_g - V_x - V_t)^2 + \frac{1}{2} (V_g - V_t)^2$$

$$V_x = (V_g - V_t) \pm \sqrt{(V_g - V_t)^2 - \frac{2I_d}{\mu_n WC_{ox}} x}$$

$$V_x = (V_g - V_t) - \sqrt{(V_g - V_t)^2 - \frac{2I_d}{\mu_n WC_{ox}} x} \quad \text{because of } V_x < V_g - V_t$$
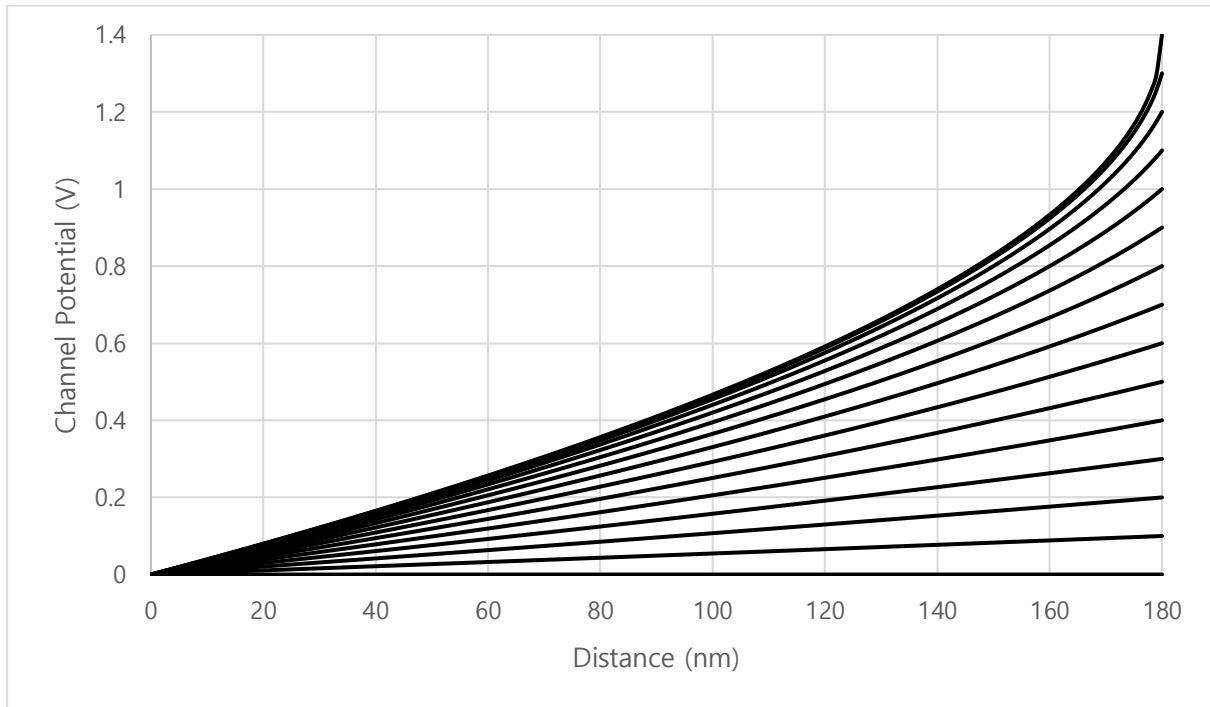
$$V_x = (V_g - V_t) - \sqrt{(V_g - V_t)^2 - \frac{2(V_g - V_t)V_{ds} - V_{ds}^2}{L} x}$$



This graph shows the relationship between channel potential and distance at  $V_{ds} = 0V$  to  $1.4V$ .