

---

# DIC L3: Introduction (3)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology



# 1.4. CMOS logic (3)

- CMOS NAND
  - If either input  $A$  or  $B$  is 0, at least one of the NMOSFETs will be OFF, breaking the path from  $Y$  to GND.

$A$	$B$	$Y$ $= A \text{ NAND } B$
0	0	1
0	1	1
1	0	1
1	1	0

 


Fig. 1.12(a)



# 1.4. CMOS logic (4)

- Series and parallel
  - NMOS: 1 = ON
  - PMOS: 0 = ON
  - Series: Both must be ON.
  - Parallel: Either can be ON.
- Conduction complements
  - Pull-up  $\leftrightarrow$  pull-down

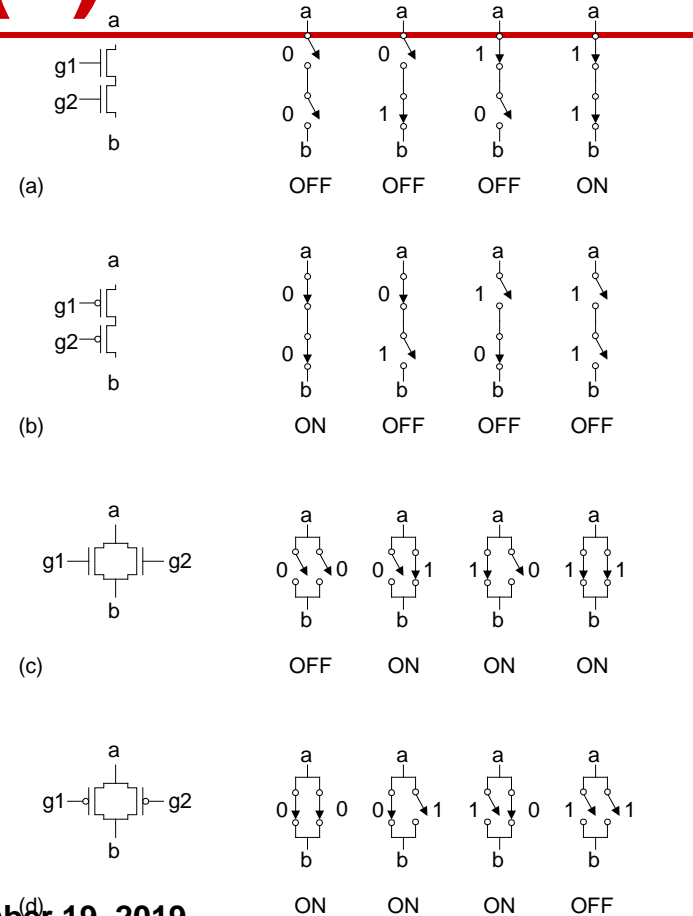


Fig. 1.15



# 1.4. CMOS logic (5)

- CMOS NOR
- Example 1.1
  - Sketch a 3-input CMOS NOR gate.
- Example 1.2
  - Sketch a static CMOS gate computing  $Y = \overline{(A + B + C)} \cdot D$


 


Fig. 1.16(a)

# 1.4. CMOS logic (6)


---

- The answer of Example 1.2

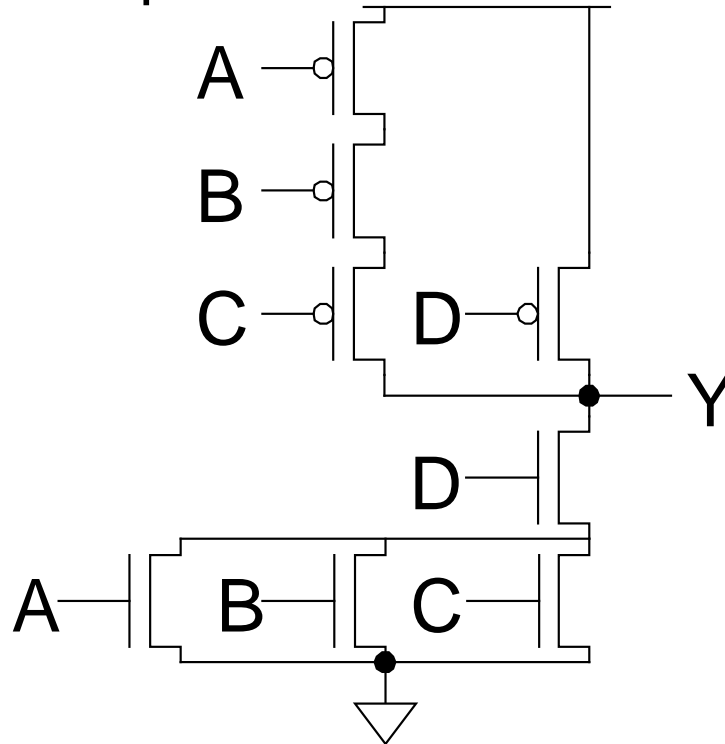


# 1.5. CMOS fabrication (1)

- Inverter cross-section

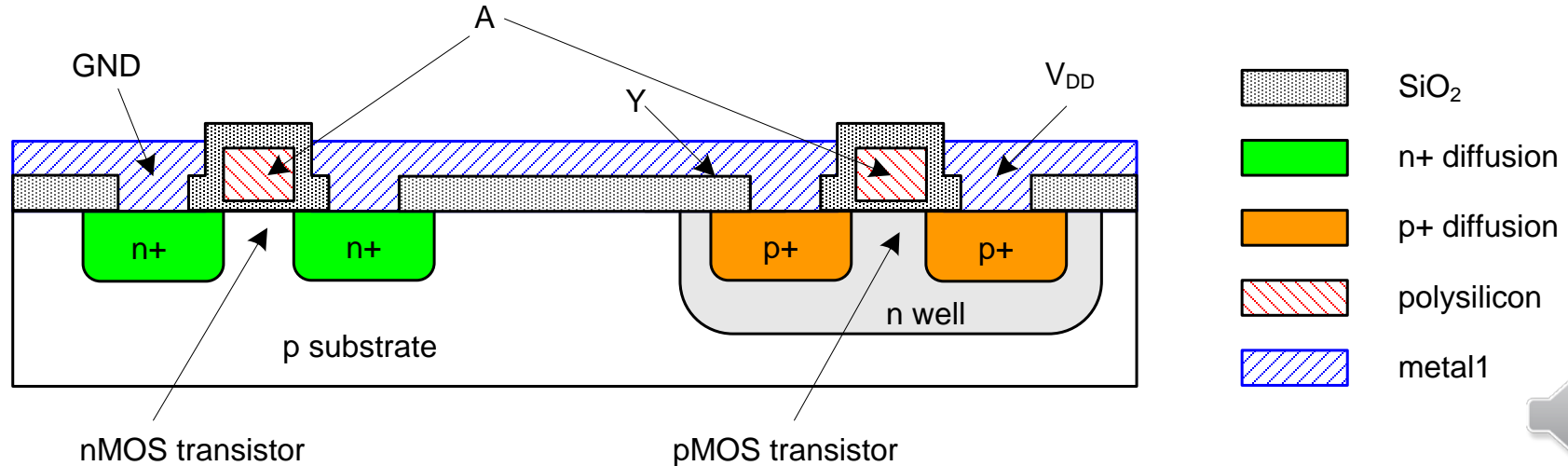

# 1.5. CMOS fabrication (2)

- Well and substrate taps

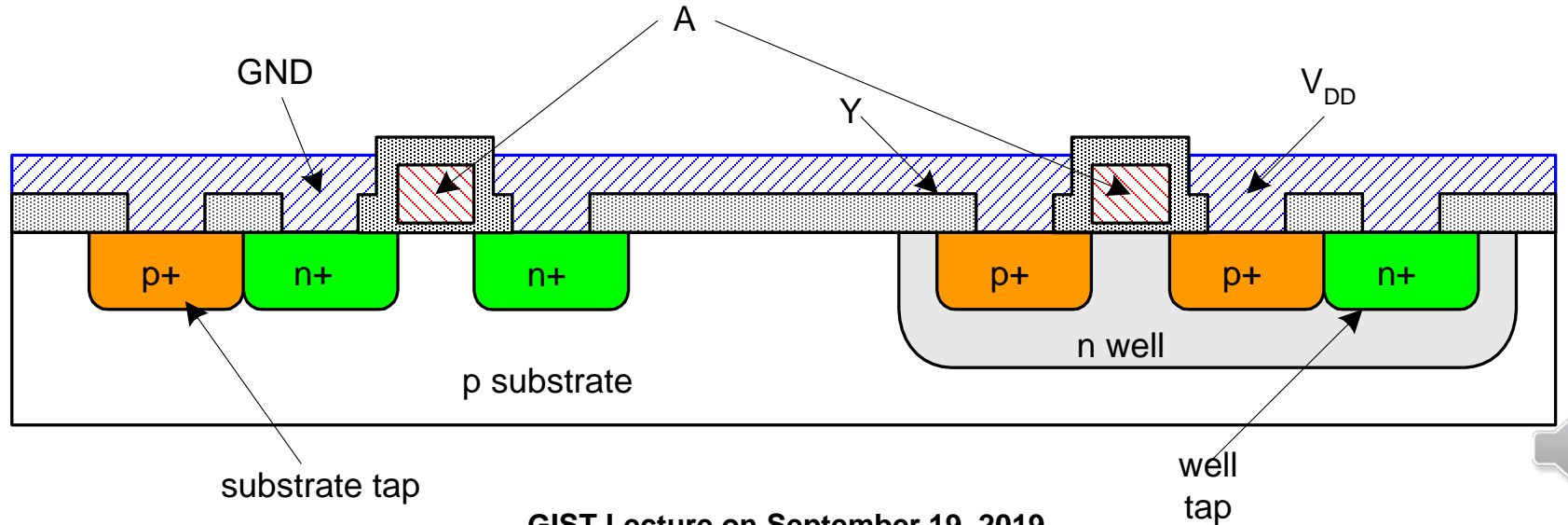

# 1.5. CMOS fabrication (3)

---

- Semiconductor process steps (Example: 0.35  $\mu\text{m}$ )
  - Well implant
  - Gate oxide
  - Poly deposition
  - Gate patterning
  - LDD implantation
  - Nitride spacer
  - Source/drain implantation





# 1.5. CMOS layout (1)

- Inverter cross-section

