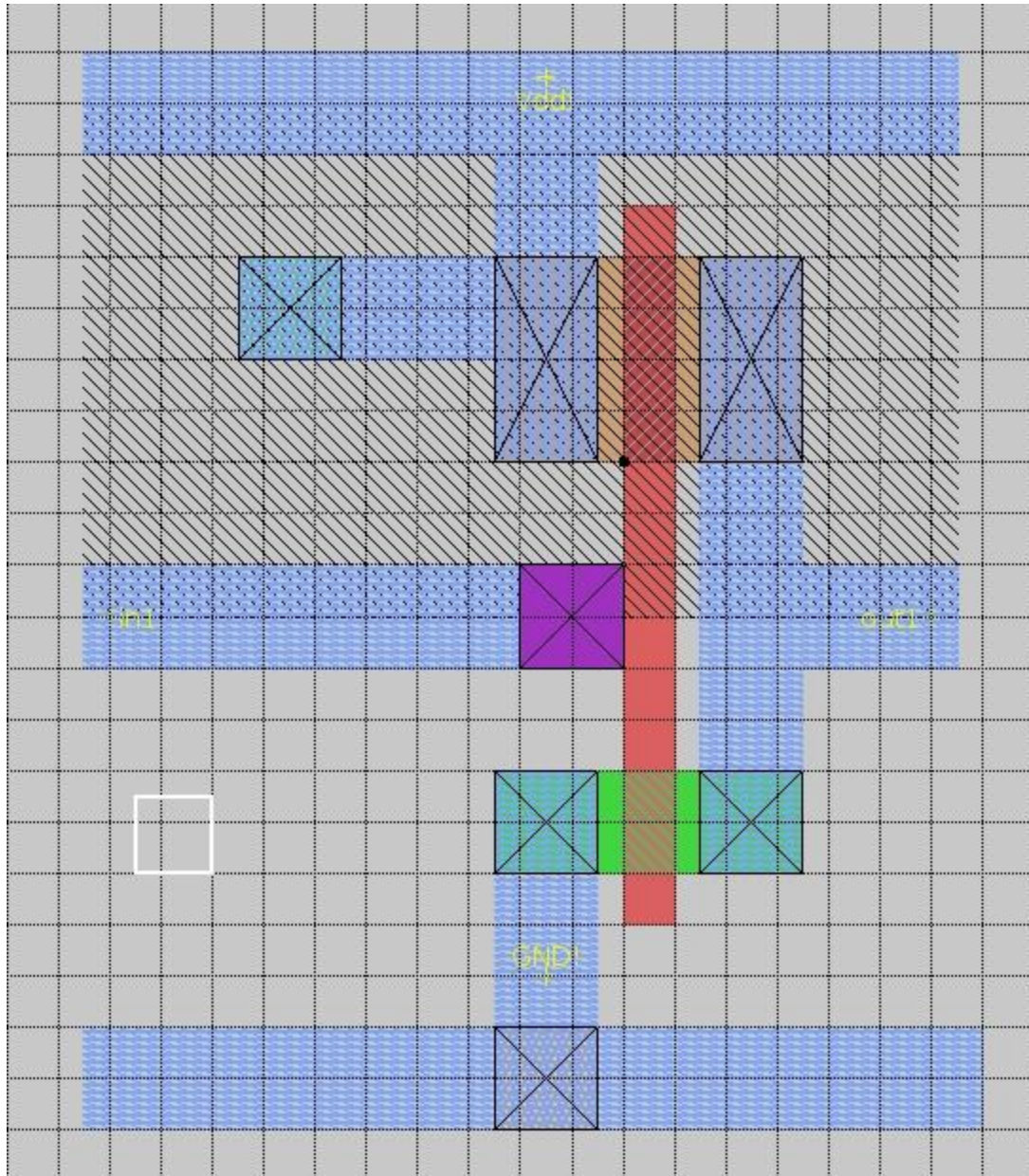


DIC HW1

20175186 최지호



* SPICE3 file created from practice1.ext - technology: scmos

.option scale=1u

M1000 out1 in1 Vdd Vdd pfet w=8 l=2

+ ad=40 pd=26 as=40 ps=26

M1001 out1 in1 GND Gnd nfet w=4 l=2

+ ad=20 pd=18 as=20 ps=18

C0 in1 Vdd 4.6fF

C1 in1 gnd! 4.6fF

C2 Vdd gnd! 3.2fF