
DIC L3: Introduction (3)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

1.4. CMOS logic (3)

- CMOS NAND
 - If either input A or B is 0, at least one of the NMOSFETs will be OFF, breaking the path from Y to GND.

A	B	Y $= A \text{ NAND } B$
0	0	1
0	1	1
1	0	1
1	1	0

 


Fig. 1.12(a)

1.4. CMOS logic (4)

- Series and parallel
 - NMOS: 1 = ON
 - PMOS: 0 = ON
 - Series: Both must be ON.
 - Parallel: Either can be ON.
- Conduction complements
 - Pull-up \leftrightarrow pull-down

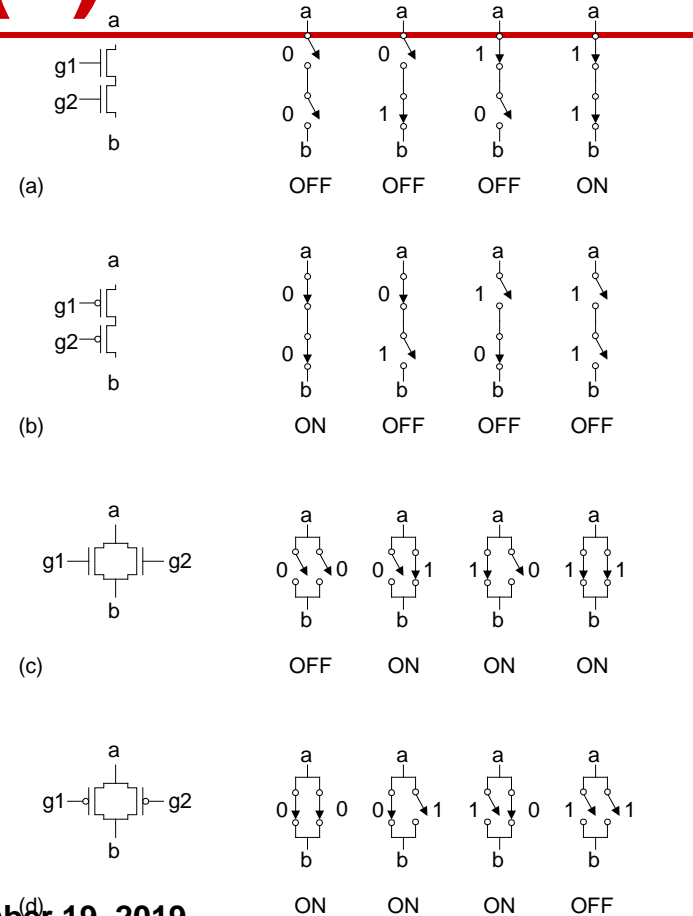


Fig. 1.15

1.4. CMOS logic (5)

- CMOS NOR
- Example 1.1
 - Sketch a 3-input CMOS NOR gate.
- Example 1.2
 - Sketch a static CMOS gate computing $Y = \overline{(A + B + C)} \cdot D$


 


Fig. 1.16(a)


1.4. CMOS logic (6)

- The answer of Example 1.2

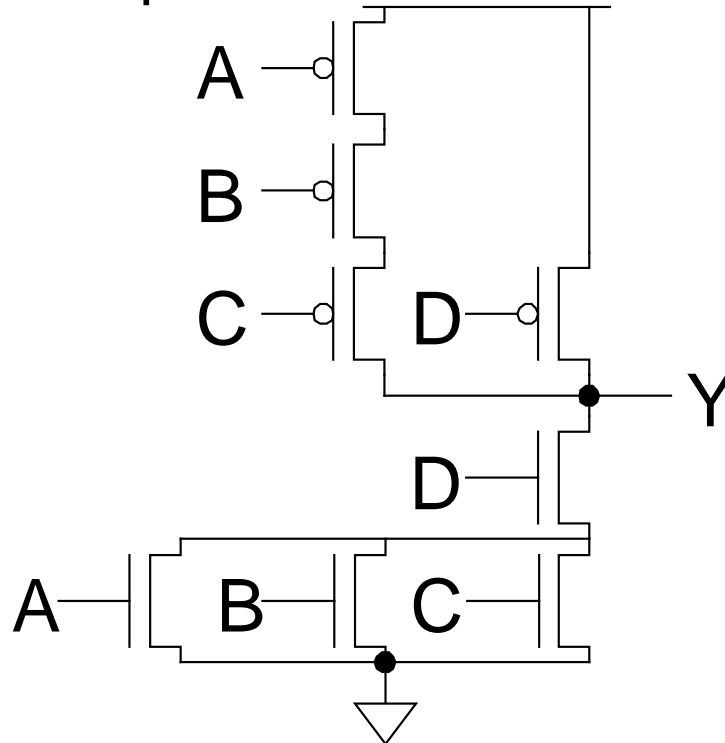


1.5. CMOS fabrication (1)

- Inverter cross-section

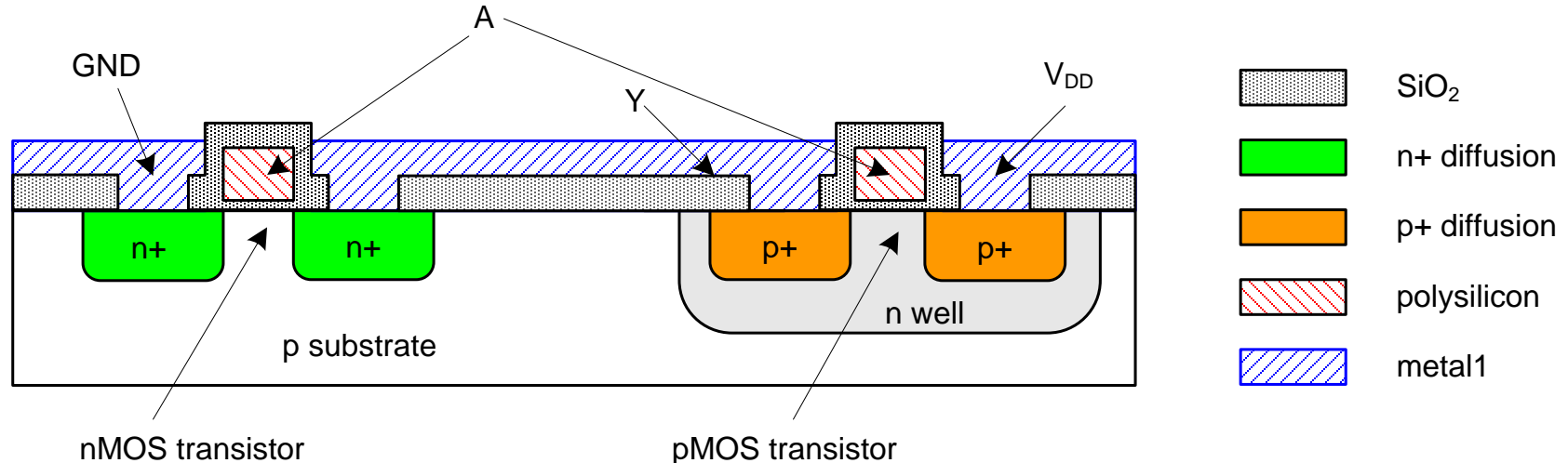

1.5. CMOS fabrication (2)

- Well and substrate taps

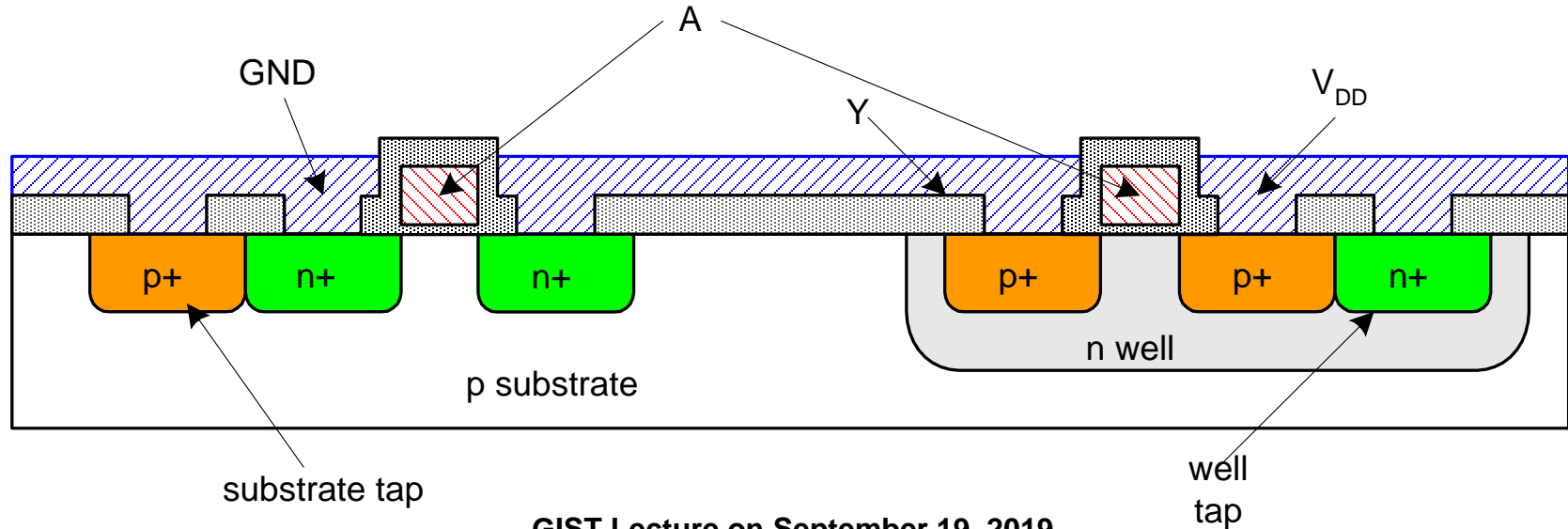

1.5. CMOS fabrication (3)

- Semiconductor process steps

1.5. CMOS layout (1)

- Inverter cross-section

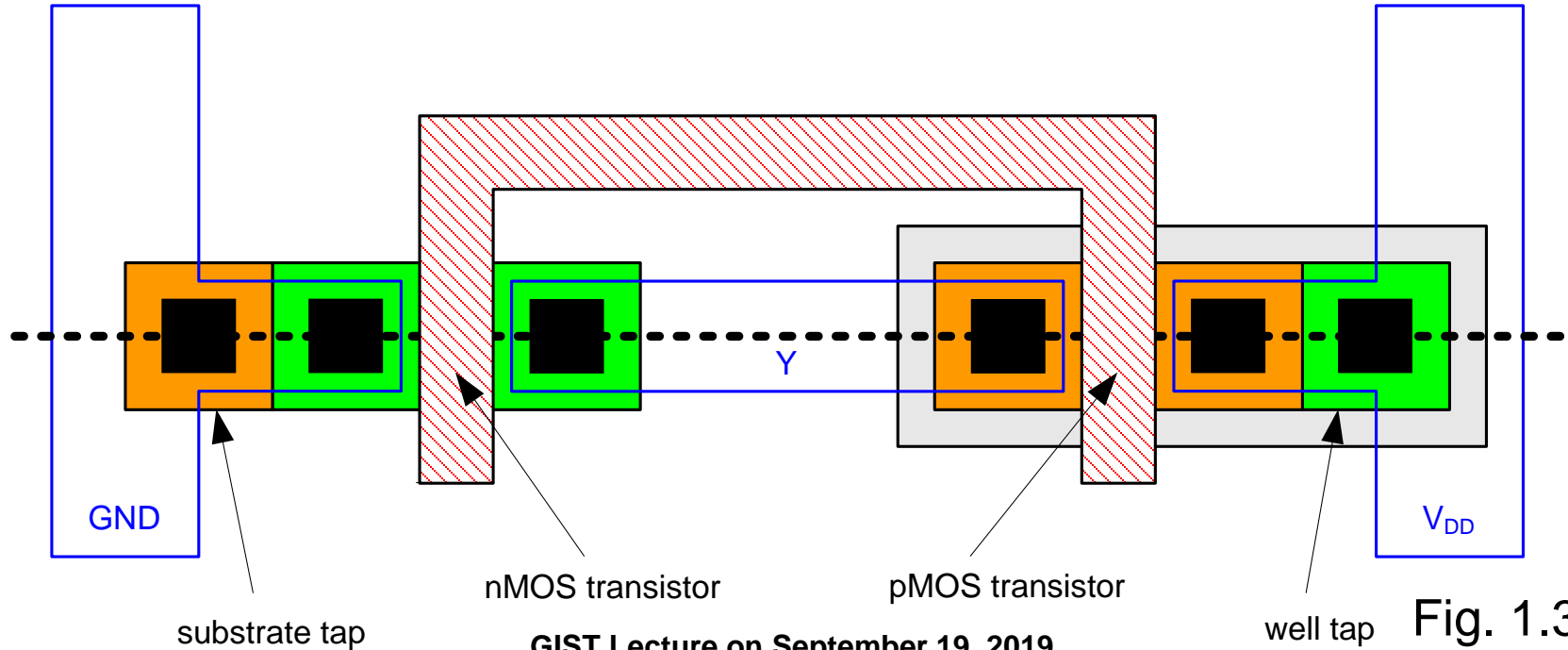


Fig. 1.35(a)

1.5. CMOS layout (2)

- Detailed mask views

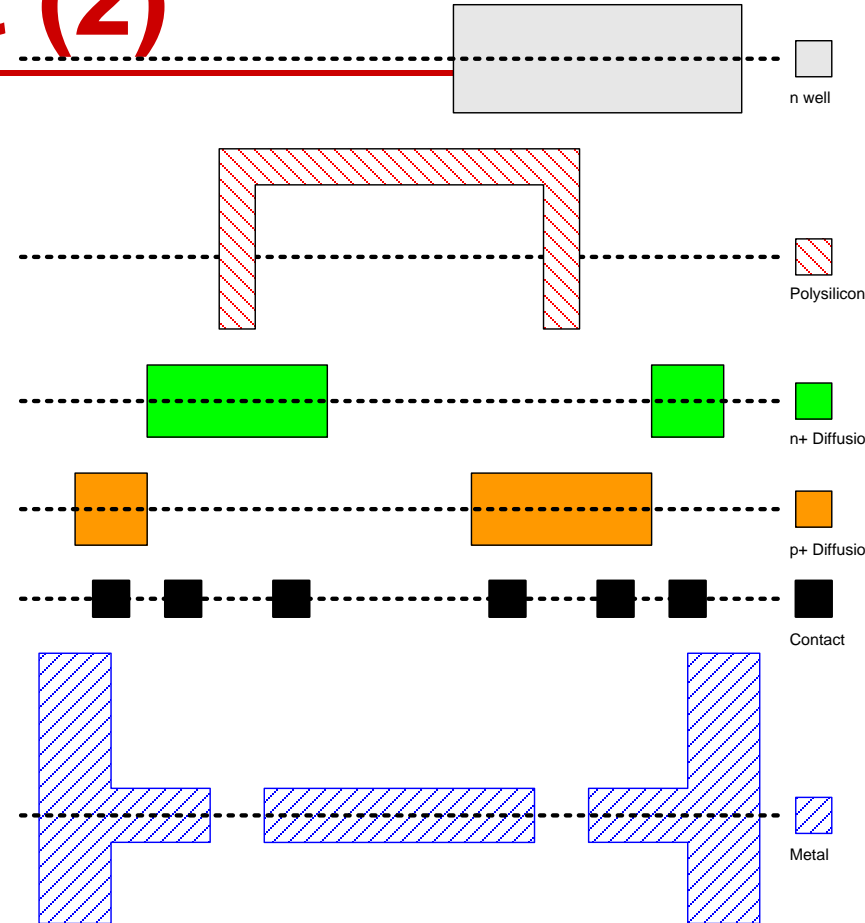


Fig. 1.35(b)-(g)

1.5. CMOS layout (3)

- Design rules in the textbook

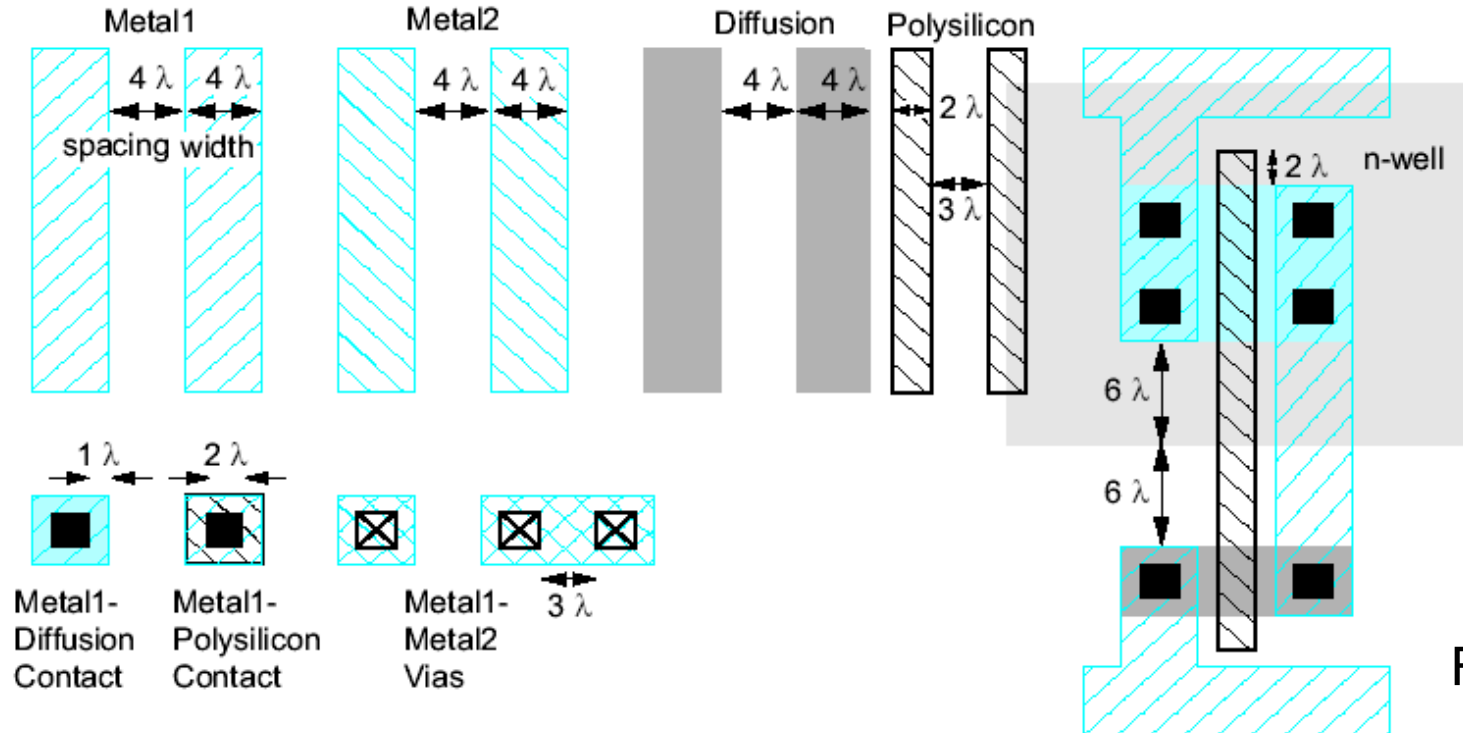


Fig. 1.39

1.5. CMOS layout (4)

- Inverter layout

 
 
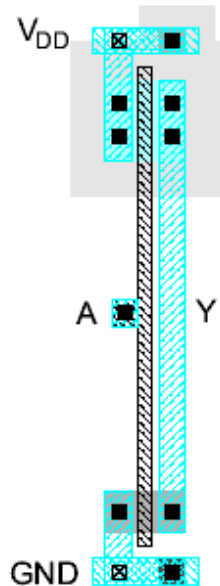


Fig. 1.40