
DIC L2: Introduction (2)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology



1.3. MOS transistors (6)

- PMOS
 - Similar, but doping and voltages are reversed.
 - Body is tied to V_{DD} .
 - V_{GS} is negative.

Metal (Polysilicon gates are gone.)


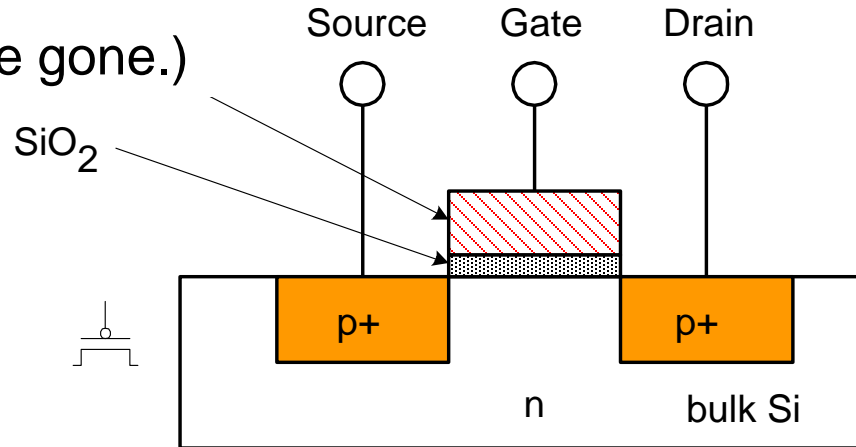


Fig. 1.9(b)

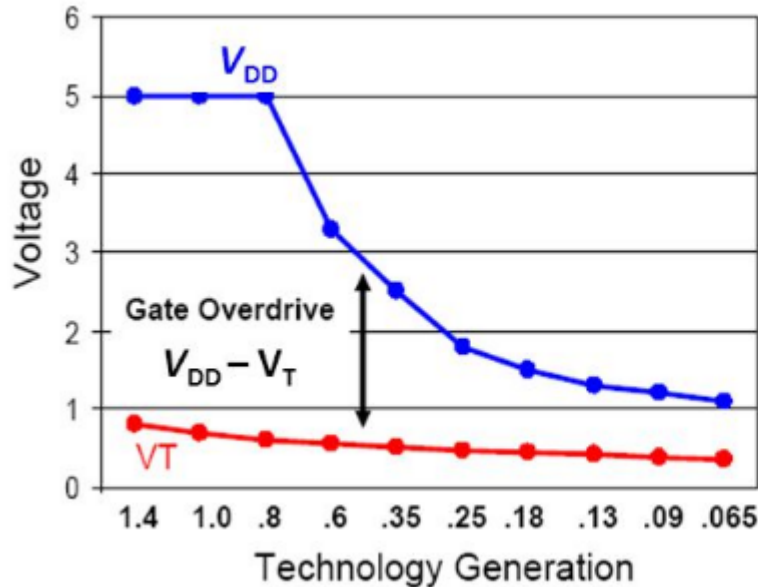1.3. MOS transistors (7)

- Power supply voltage
 - In 1980's, V_{DD} was 5 V.
- IEDM(or VLSI) papers
 - 130nm: 2000
 - 90nm: 2003
 - 65nm: 2004
 - 45nm: 2007
 - 32nm: 2008
 - 22nm: 2012
 - 14nm (or 16nm): 2014



Source: P. Packan (Intel),
2007 IEDM Short Course



1.3. MOS transistors (8)

- Transistors as switches
 - V_G controls path from source to drain.

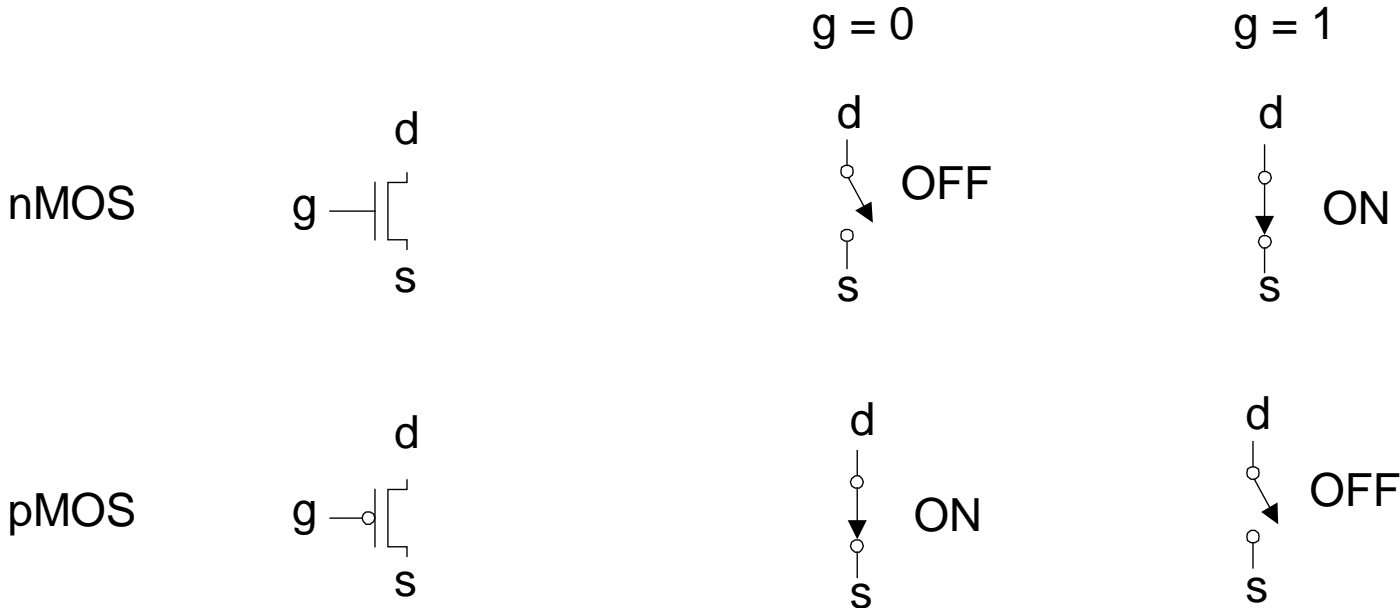


Fig. 1.10

1.4. CMOS logic (1)

- CMOS inverter
 - When the input A is 0, the NMOS transistor is OFF and the PMOS transistor is ON.
 - Thus, the output Y is pulled up to 1.

A	$Y = \text{NOT } A$
0	1
1	0

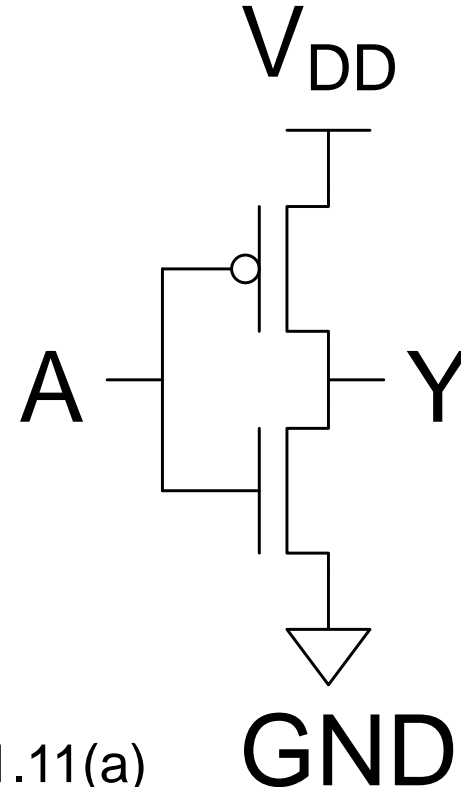


Fig. 1.11(a)



1.4. CMOS logic (2)

- Complementary CMOS gates
- Pull-down and pull-up networks
 - NMOS pull-down
 - PMOS pull-up

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z	1
Pull-down ON	0	Crowbarred (X)

