
DIC L2: Introduction (2)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

1.3. MOS transistors (6)

- PMOS

- Similar, but doping and voltages are reversed.
- Body is tied to V_{DD} .
- V_{GS} is negative.

Metal (Polysilicon gates are gone.)


 


Fig. 1.9(b)

 1.3. MOS transistors (7)

- Power supply voltage MOS
 - In 1980's, V_{DD} was 5 V.
- IEDM(or VLSI) papers
 - 130nm: 2000
 - 90nm: 2003
 - 65nm: 2004
 - 45nm: 2007
 - 32nm: 2008
 - 22nm: 2012
 - 14nm (or 16nm): 2014



Source: P. Packan (Intel),
2007 IEDM Short Course

1.3. MOS transistors (8)

- Transistors as switches
 - V_G controls path from source to drain.

 


Fig. 1.10

1.4. CMOS logic (1)

- CMOS inverter
 - When the input A is 0, the NMOS transistor is OFF and the PMOS transistor is ON.
 - Thus, the output Y is pulled up to 1.

A	$Y = NOT A$
0	1
1	0

 


Fig. 1.11(a)

1.4. CMOS logic (2)

- CMOS NAND
 - If either input A or B is 0, at least one of the NMOSFETs will be OFF, breaking the path from Y to GND.

A	B	Y $= A \text{ NAND } B$
0	0	1
0	1	1
1	0	1
1	1	0


 


Fig. 1.12(a)

1.4. CMOS logic (3)

- Complementary CMOS gates
- Pull-down and pull-up networks
 - NMOS pull-down
 - PMOS pull-up

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z	1
Pull-down ON	0	Crowbarred (X)

 

1.4. CMOS logic (4)

- CMOS NOR
- Example 1.1
 - Sketch a 3-input CMOS NOR gate.
- Example 1.2
 - Sketch a static CMOS gate computing $Y = \overline{(A + B + C)} \cdot D$


 


Fig. 1.16(a)


1.5. CMOS fabrication (1)

- Inverter cross-section

 

1.5. CMOS fabrication (2)

- Well and substrate taps

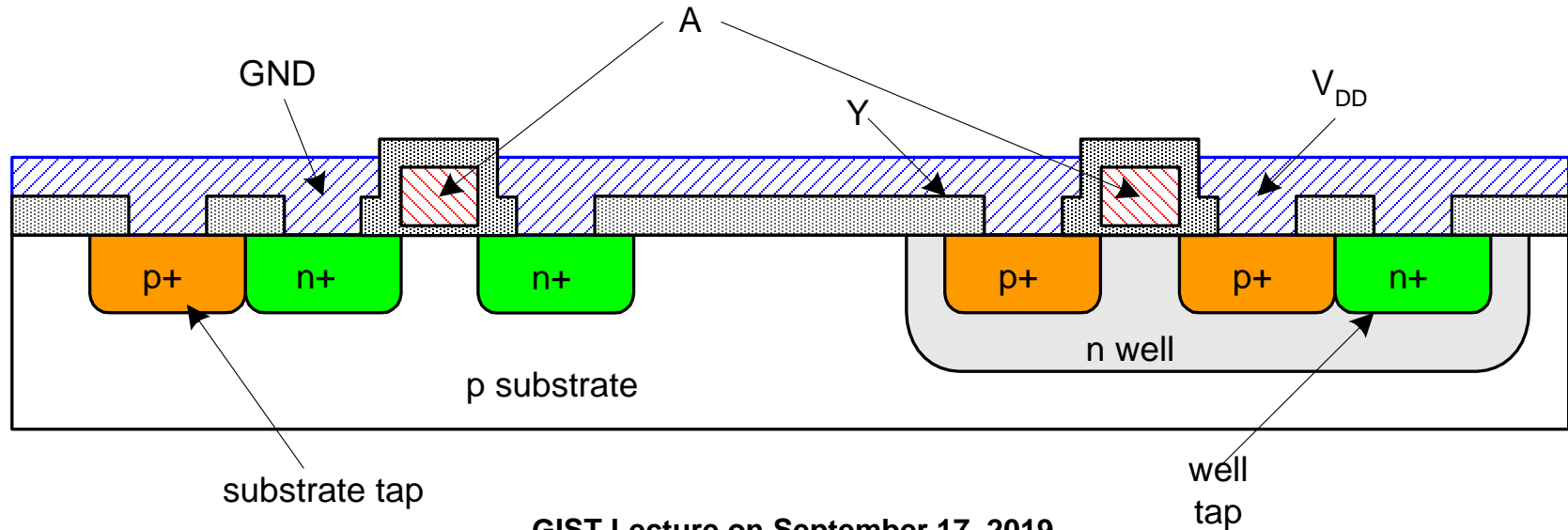

1.5. CMOS fabrication (3)

- Semiconductor process steps

1.5. CMOS layout (1)

- Inverter cross-section

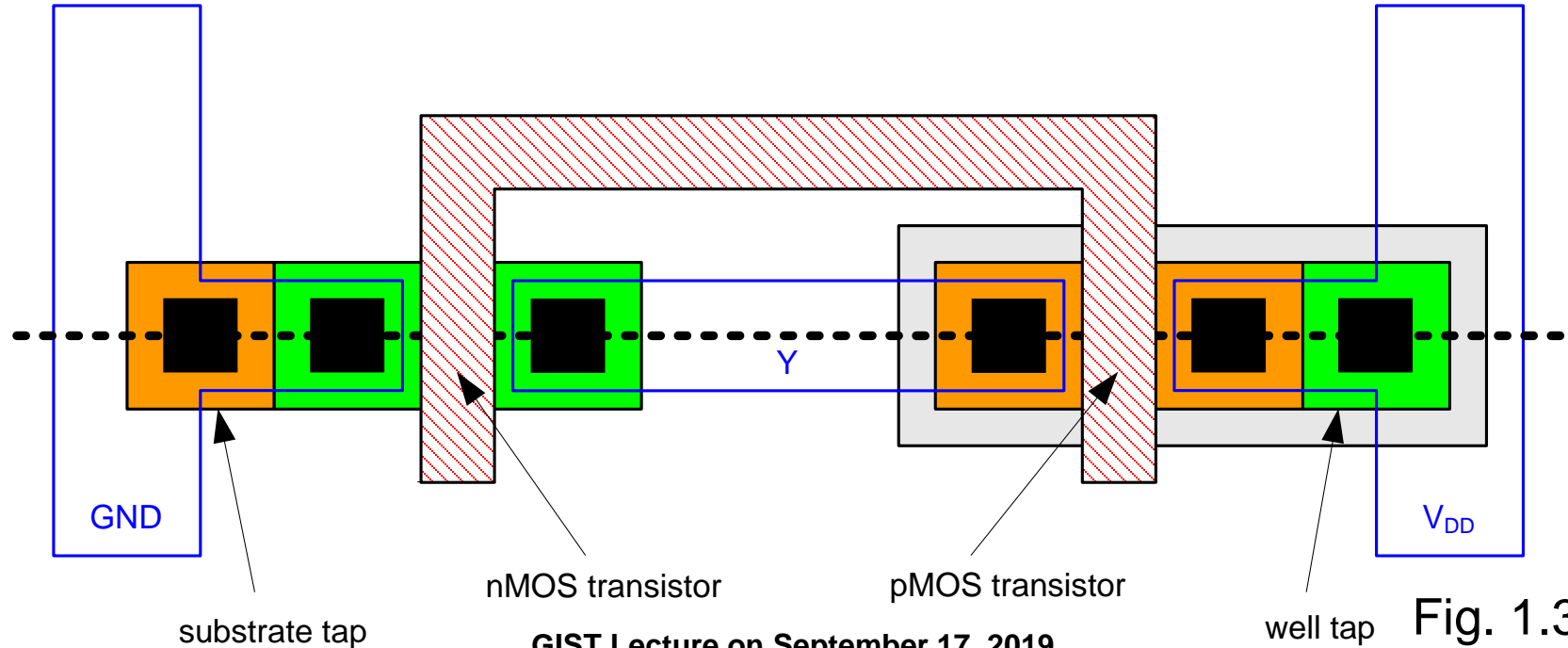


Fig. 1.35(a)

1.5. CMOS layout (2)

- Detailed mask views

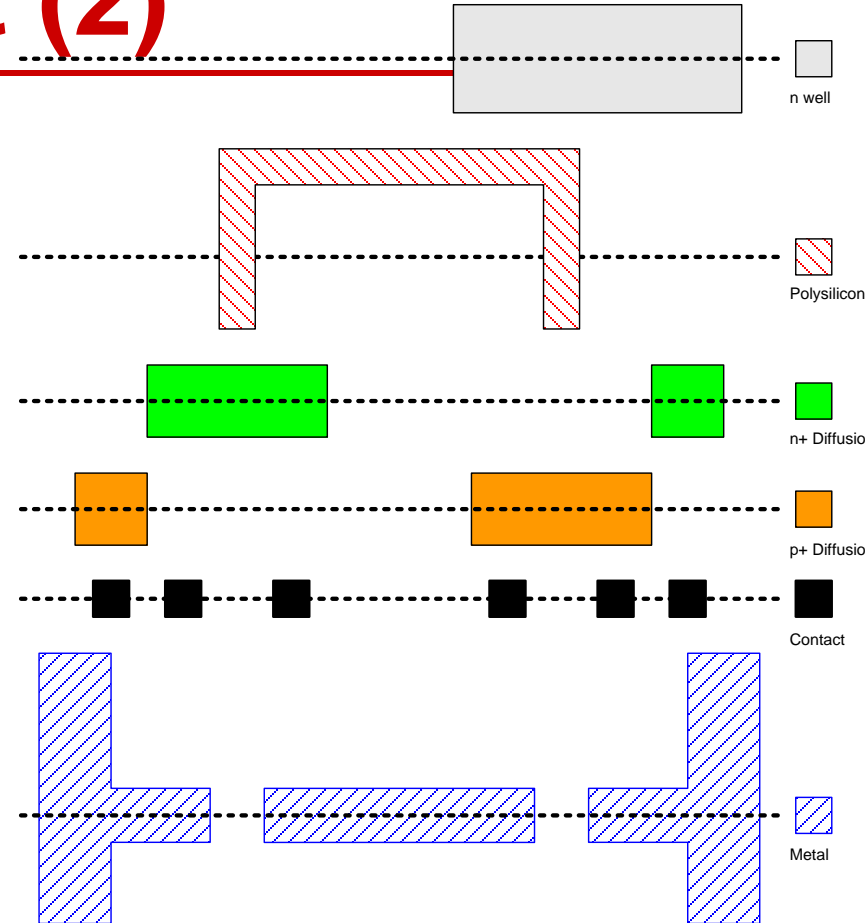


Fig. 1.35(b)-(g)

1.5. CMOS layout (3)

- Design rules in the textbook

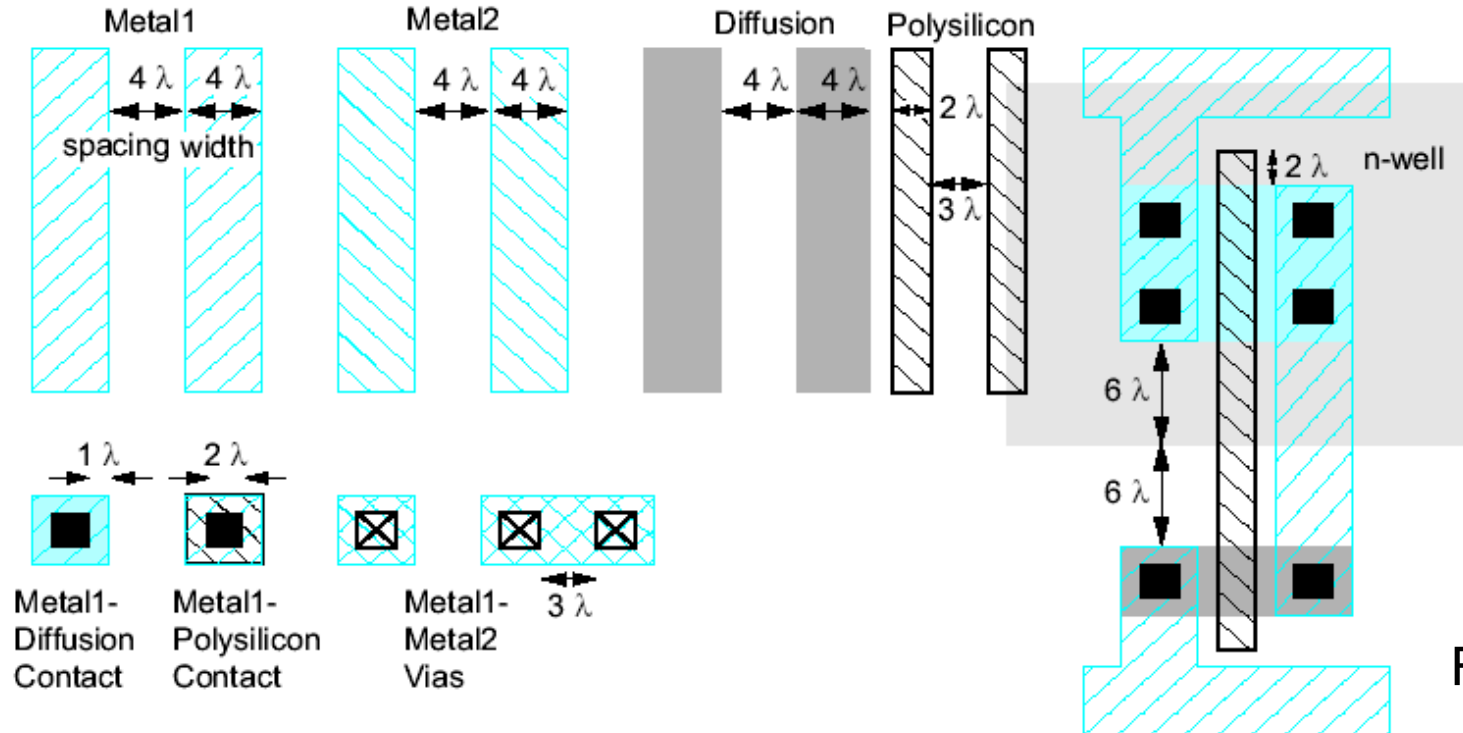


Fig. 1.39

1.5. CMOS layout (4)

- Inverter layout

 
 
 


Fig. 1.40