
 


HW 2


Ju Hyung Lee
20194072

 

[Example 1] I observed some delay from capacitor in RC circuit simulation. Although input voltage V_{in} increases linearly during 0.1 ns to 0.15 ns, exponential response of output voltage V_{out} was observed.



 [Example 2] Saturation of drain current at sufficiently high drain-source voltage V_{DS} was observed for each gate voltage. According to simulation results, higher gate voltage implies higher drain current.



[Example 3] Input voltage V_{in} was inverted to output voltage V_{out} , so that slope of the output voltage had different sign to the input. Also, output voltage had some transition characteristic around 2.5 V of input voltage.